

73 Magazine

for Radio Amateurs

- 28 **Five-Chip Auto IDer**
—in case you forget..... Bartholomew
- 29 **The Vacationer**
—B&W's portable antenna..... WA2ALT
- 30 **Tone Decoder Improvements**
—another step toward perfection..... WA1LMV
- 32 **The All-Wrong Power Supply**
—works in spite of itself..... WA3EEC
- 33 **The Hardhearted Rf Detector**
—insensitive to harmonics..... N4ES
- 34 **Custom-Designed Power Supplies**
—try the 723..... K2GEJ
- 39 **A Touch of Class**
—nifty \$35 operating console..... WA4CUD
- 40 **How To Bury Coax**
—the garden cultivator technique..... W4MEA
- 42 **Mobile Antenna Ingenuity**
—cheap HF radiators..... WA8ATE
- 46 **Impedance and Other Ogres**
—another look at swr..... Staff
- 50 **The Active Filter Cookbook**
—review of Lancaster's treatise..... VE2BVW
- 52 **A Rock-Solid AFSK Oscillator**
—hooray for stability!..... WB4MBL
- 54 **Pulser Plus**
—a one-shot with more..... VE2BVW
- 56 **Oh, My Poor Quad!**
—measuring wind speed..... K2CL
- 58 **A Self-Contained, Fully-Automated,
Transistorized Fuse Tester**
—amaze your friends..... G3TAI
- 60 **Don't Get Burgled!**
—build this simple alarm..... Fletcher
- 61 **Power x 2**
—dual auto batteries..... Miller
- 62 **Experimenting with Tones**
—fun with functions..... W2FPP
- 64 **Synthesize Your Ash Tray**
—article for non-smokers..... WB9VWM
- 66 **Attention, Satellite Watchers!**
—a solid-state monitor for GOES..... WB8DQT
- 78 **Batteries Dead?**
—take preventative measures..... Staff
- 80 **How to Nab a Jammer**
—another use for 220..... WB0CMC
- 84 **This Station Plays Beautiful CW**
—with a Morse keyboard..... WB9WRE
- 92 **The Cure for Migraines**
—a low-pass CW filter..... Harper
- 94 **IO An 8080 Repeater Control System**
—part I: an overview..... N3IC
- 106 **IO The Cosmac Connection: Part 2**
—meeting Mr. Morse..... VE3CWY
- 110 **IO Learning the Code**
—a better way..... Waldie
- 116 **IO Books for Beginners**
—you have to start somewhere!..... WA7NEV
- 118 **The 2 Meter ECM Caper**
—James Bond, move over!..... W2JTP
- 120 **"I Love My Ten-Tec!"**
—a look at the 540/544..... WA0JIH
- 122 **A \$5 Phone Patch**
—the darn thing really works..... WA6RJK
- 136 **The Filcher Foiler Revisited**
—vehicular protection..... Davis
- 137 **Build An Economy Zener Checker**
—versatile test rig..... W4RBL
- 140 **Alaskan Adventure**
—stalking the elusive KL7..... WB5WDG
- 142 **The Last DXpedition**
—"QTH hr is Purgatory"..... K3FDL
- 144 **An Audio Morse Memory**
—got a tape recorder?..... WB6WQN
- 146 **The Amazing Active Attenuator**
—can you find a use for it?..... VE2BVW
- 148 **A Single IC Time Machine**
—amazing clock..... K6SK
- 156 **Car Battery Charger**
—junk-box special..... W1DWZ
- 160 **Immortality for Vacuum Tubes?**
—build a solid state tube saver..... K5KXM
- 163 **The Hot Mugger X1**
—coffee drinkers, rejoice..... WB9QZE
- 164 **Build the Mini-Probe**
—it's only logical..... Rister

must have only *one* low tone and only *one* high tone.

The next section of the valid-digit recognizer is the delay circuit consisting of U3, U4, and U5. R1 and C1 determine the time delay. The output of the valid-digit recognizer circuitry is U3, pin 3. Pin 3 of U3 goes low only when one low tone AND only one high tone are present and they must remain uninterrupted for the time duration set by R1 and C1. Optimum setting of R1 is from 0.25 to 0.5 seconds. This setting may vary for your particular setup. As a rule of thumb, set R1 to be fast enough for your signaling requirements, but slow enough to reject erratic pulsing. Remember that a condition could exist where a certain voice may be decoded as two tones which happen to be two touchtone™ frequencies.

This would meet the requirements of only one low and only one high tone, but would not be decoded if R1 were set correctly.

Next, we use the output of the valid-digit recognizer to gate the outputs of the 567s into the eight-to-sixteen-line decoder. U5 and U6 are 7414 Schmitt triggers. They will further condition the outputs of the 567s and shape the out-

put waveform. U7 and U8 (7400 NAND gates) provide the gating of the 567s to the sixteen-line decoder. Thus, no tone decoding can take place without valid-digit recognition because the outputs of the 567s are not being applied to the sixteen-line decoder unless valid-digit recognition has occurred. The outputs of the sixteen-line decoder, U9-U12 (7402s), are normally low and go

high when the digit is decoded.

The system described here is in use at three repeaters in the Hartford CT area (WR1ABM: .28/.88 and 442.85-447.85 and WR1AFU: .75/.15) as autopatch and control decoders and are working well without any problems. With a 0.5-second response time, there has never been a false activation of any function. ■

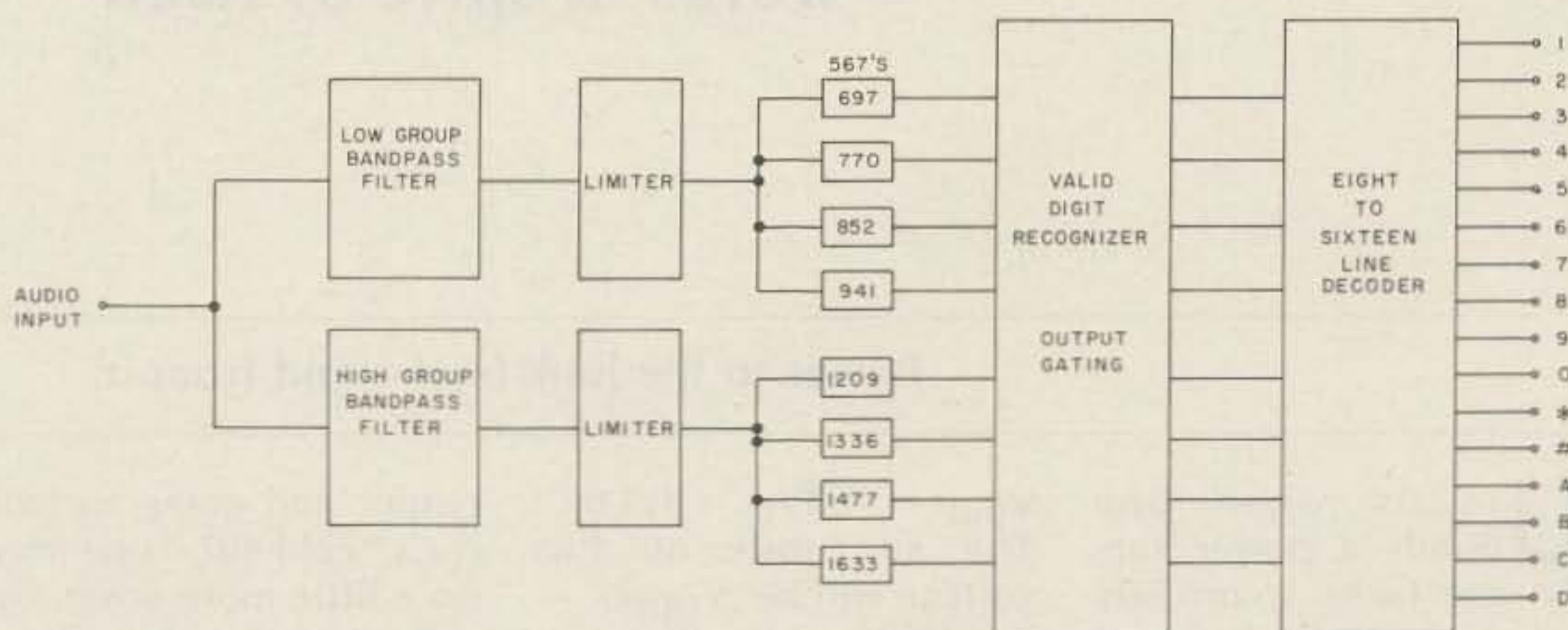



Fig. 2. Block diagram of decoding system.

POWERFUL KEN PRO ROTATORS



«SWISS QUAD VHF SERIES»

Multi Band Beam Super DX Series

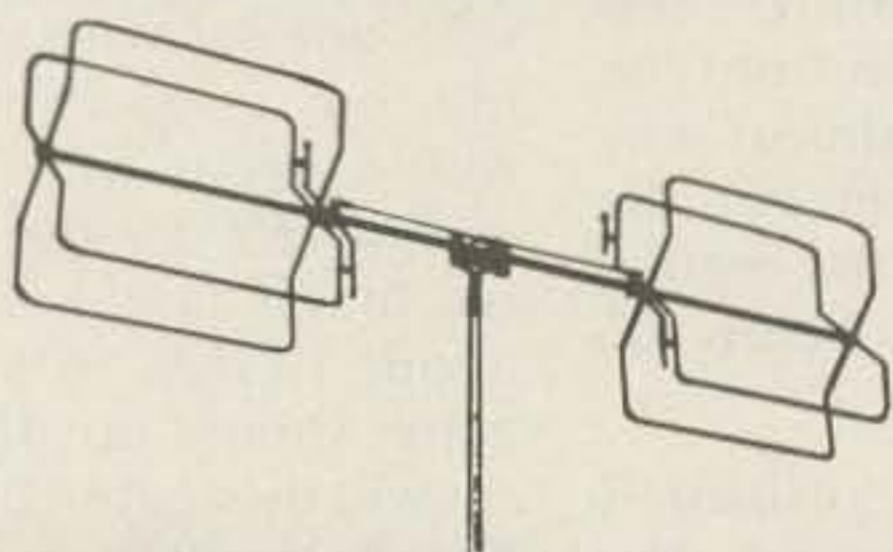

SQ-22 TWO METER DUAL QUAD


ANTENNA GAIN AND FRONT TO-BACK RATIO ARE WELL IMPROVED WHEN TWO ELEMENTS ARE DRIVEN AT ONE TIME WITH PHASE DIFFERENCE COMPARED TO A SINGLE DRIVEN ELEMENT SUCH AS A CONVENTIONAL QUAD OR YAGI. THE SQ-22 PROVIDES THE OWNER WITH SUCH FEATURES. SIMPLE ASSEMBLY AND LIGHT WEIGHT.

THE 3F35DX BEAM IS FOR USE IN THE 10, 15 AND 20 METER AMATEUR BANDS. THIS IS A HIGH PERFORMANCE BEAM THAT MAKES USE OF A COMBINATION OF PARALLEL FEED, FULL SIZE INDIVIDUAL DRIVEN ELEMENTS FOR EACH BAND. ALONG WITH THE USE OF HI-Q PARASITIC TRAPPED ELEMENTS. HIGH POWER RATING 3KW AND EXCELLENT VSWR ON EACH BAND.

WRITE OR CALL FOR PRICES AND INFORMATION.

DEALER INQUIRIES WELCOME

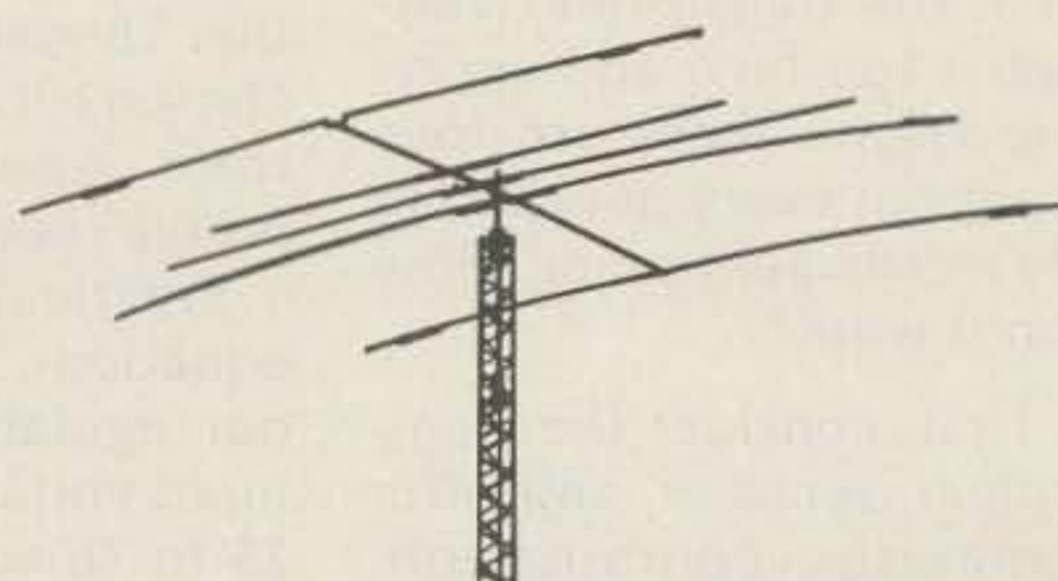ALL ANTENNAS IN STOCK, FOB OKLAHOMA CITY, OKLA.



3F35DX MULTI BAND FIVE ELEMENT BEAM

BRODIE ELECTRONICS COMPANY

2537 Edgewood Drive
Moore, Oklahoma 73160
405-794-0406

✓ B42